

# Kogge-Stone Adder: Working and Algorithm

## Introduction

The Kogge-Stone adder is a parallel prefix adder that performs binary addition with logarithmic depth, making it one of the fastest adder architectures available. It trades area for speed by using more hardware to achieve minimal delay, making it ideal for high-performance computing applications.

## Working Principle

The Kogge-Stone adder is based on the parallel prefix computation of carry signals. Instead of waiting for carries to ripple through sequentially like in a ripple carry adder, it computes all carries in parallel using a tree-like structure.

## Key Concepts

**Generate (G):**  $G_i = A_i \cdot B_i$

- Position  $i$  generates a carry regardless of the input carry
- This occurs when both input bits are 1

**Propagate (P):**  $P_i = A_i \oplus B_i$

- Position  $i$  propagates a carry from the previous position
- This occurs when exactly one input bit is 1

**Carry:**  $C_i = G_i + P_i \cdot C_{i-1}$

- The carry output depends on either generating a carry or propagating the previous carry

The adder computes carry signals by combining generate and propagate signals across different spans using the parallel prefix operation.

## Algorithm

The Kogge-Stone algorithm operates in three main phases:

### Phase 1: Initialization

For each bit position  $i$  (from 0 to  $n-1$ ):

- Calculate initial Generate:  $G[i,i] = A_i \cdot B_i$
- Calculate initial Propagate:  $P[i,i] = A_i \oplus B_i$

This creates the base level of the prefix tree with individual bit positions.

## Phase 2: Parallel Prefix Computation

For each level  $k$  from 1 to  $\lceil \log_2(n) \rceil$ : For each position  $i$  where the operation is applicable: -  $G[i,j]$   
 $= G[i,k] + P[i,k] \cdot G[k-1,j] - P[i,j] = P[i,k] \cdot P[k-1,j]$

This creates a tree structure where:

- Each level doubles the span of the prefix computation
- Level  $k$  can look back  $2^k$  positions
- The tree has logarithmic depth

## Phase 3: Sum Generation

For each bit position  $i$ :

- Sum  $S_i = P_i \oplus C_{i-1}$
- Where  $C_{i-1}$  is derived from the computed  $G$  and  $P$  values
- $C_{-1} = 0$  (no initial carry input)

# Detailed Algorithm Steps for n-bit Addition

## Step 1: Input Processing

- Take two  $n$ -bit numbers  $A = (A_{n-1}, A_{n-2}, \dots, A_1, A_0)$  and  $B = (B_{n-1}, B_{n-2}, \dots, B_1, B_0)$
- Initialize carry input  $C_{-1} = 0$

## Step 2: Initial G and P Computation

For  $i = 0$  to  $n-1$ :

$$G[0][i] = A_i \text{ AND } B_i$$

$$P[0][i] = A_i \text{ XOR } B_i$$

## Step 3: Tree Construction

$$\text{levels} = \text{ceil}(\log_2(n))$$

For level = 1 to levels:

$$\text{step} = 2^{\text{level}}$$

For  $i = \text{step}-1$  to  $n-1$ :

```

if (i-step/2) >= 0:
    G[level][i] = G[level-1][i] OR (P[level-1][i] AND G[level-1][i-step/2])
    P[level][i] = P[level-1][i] AND P[level-1][i-step/2]

```

#### Step 4: Carry Extraction

```

For i = 0 to n-1:
    if i == 0:
        Ci-1 = 0
    else:
        Ci-1 = G[final_level][i-1]

```

#### Step 5: Sum Calculation

```

For i = 0 to n-1:
    Si = P[0][i] XOR Ci-1

```

### Example: 4-bit Kogge-Stone Adder

Let's trace through a 4-bit addition: A = 1011, B = 0110

#### Step 1: Initialize

- A = [1,0,1,1], B = [0,1,1,0]

#### Step 2: Compute Initial G and P

- G[0] = [0,0,1,0] (A AND B for each position)
- P[0] = [1,1,0,1] (A XOR B for each position)

#### Step 3: Build Tree (2 levels for 4-bit)

##### Level 1:

- $G[1][1] = G[0][1] \text{ OR } (P[0][1] \text{ AND } G[0][0]) = 0 \text{ OR } (1 \text{ AND } 0) = 0$
- $P[1][1] = P[0][1] \text{ AND } P[0][0] = 1 \text{ AND } 1 = 1$
- $G[1][2] = G[0][2] \text{ OR } (P[0][2] \text{ AND } G[0][1]) = 1 \text{ OR } (0 \text{ AND } 0) = 1$
- $P[1][2] = P[0][2] \text{ AND } P[0][1] = 0 \text{ AND } 1 = 0$

##### Level 2:

- $G[2][3] = G[1][3] \text{ OR } (P[1][3] \text{ AND } G[1][1]) = 0 \text{ OR } (1 \text{ AND } 0) = 0$

- $P[2][3] = P[1][3] \text{ AND } P[1][1] = 1 \text{ AND } 1 = 1$

#### Step 4: Generate Sum

- $S_0 = P[0][0] \text{ XOR } 0 = 1 \text{ XOR } 0 = 1$
- $S_1 = P[0][1] \text{ XOR } G[0][0] = 1 \text{ XOR } 0 = 1$
- $S_2 = P[0][2] \text{ XOR } G[1][1] = 0 \text{ XOR } 0 = 0$
- $S_3 = P[0][3] \text{ XOR } G[2][2] = 1 \text{ XOR } 1 = 0$

Result: Sum = 0011, Carry\_out =  $G[2][3] = 1$

## Characteristics and Complexity

### Advantages

- **Logarithmic Delay:**  $O(\log n)$  propagation delay
- **Regular Structure:** Suitable for VLSI implementation
- **Predictable Timing:** No variable-length carry chains
- **High Speed:** Fastest among practical adder architectures
- **Scalable:** Performance scales well with bit width

### Disadvantages

- **High Area Cost:**  $O(n \log n)$  gates required
- **Power Consumption:** Significant due to large number of gates
- **Complex Routing:** Irregular connections increase layout complexity
- **Cost:** More expensive than simpler adder architectures

### Complexity Analysis

- **Time Complexity:**  $O(\log n)$
- **Space Complexity:**  $O(n \log n)$
- **Gate Count:** Approximately  $2n \log_2 n$  gates
- **Levels:**  $\lceil \log_2 n \rceil$  levels in the prefix tree

## Applications

The Kogge-Stone adder is particularly valuable in:

- **High-Performance Processors:** Where addition speed is critical
- **Arithmetic Logic Units (ALUs):** For fast integer operations
- **Floating-Point Units:** For mantissa addition in FP operations
- **Digital Signal Processing:** Where throughput is important

- **Cryptographic Hardware:** For modular arithmetic operations
- **Graphics Processing Units:** For parallel arithmetic operations

## Implementation Considerations

### Hardware Implementation

- Use of regular cell structures for easier layout
- Careful consideration of wire delays in deep submicron technologies
- Power optimization through clock gating and voltage scaling
- Pipeline register insertion for higher frequency operation

### Design Trade-offs

- Area vs. Speed: Kogge-Stone maximizes speed at the cost of area
- Power vs. Performance: Higher transistor count leads to increased power
- Regularity vs. Optimality: Some optimization possible but reduces regularity

## Conclusion

The Kogge-Stone adder represents an optimal solution for applications requiring the fastest possible binary addition. While it consumes more area and power compared to simpler adders, its logarithmic delay makes it indispensable in high-performance computing systems where addition speed is the primary constraint. The regular tree structure and predictable timing characteristics make it a popular choice in modern processor designs despite the increased hardware complexity.

# Verilog Code

```
1 module kogge_stone_4bit (  
2     input  [3:0] a,      // 4-bit input A  
3     input  [3:0] b,      // 4-bit input B  
4     input          cin,  // Carry input  
5     output [3:0] sum,    // 4-bit sum output  
6     output          cout // Carry output  
7 );  
8  
9 // Internal signals for Generate and Propagate  
10 wire [3:0] g0, p0;      // Level 0 (initial G and P)  
11 wire [3:0] g1, p1;      // Level 1  
12 wire [3:0] g2, p2;      // Level 2  
13 wire [3:0] c;           // Carry signals  
14  
15 // Level 0: Initial Generate and Propagate computation  
16 assign g0[0] = a[0] & b[0];  
17 assign g0[1] = a[1] & b[1];  
18 assign g0[2] = a[2] & b[2];  
19 assign g0[3] = a[3] & b[3];  
20  
21 assign p0[0] = a[0] ^ b[0];  
22 assign p0[1] = a[1] ^ b[1];  
23 assign p0[2] = a[2] ^ b[2];  
24 assign p0[3] = a[3] ^ b[3];  
25  
26 // Level 1: Span of 2  
27 // Position 0: No change (base case)  
28 assign g1[0] = g0[0];  
29 assign p1[0] = p0[0];  
30  
31 // Position 1: Look back 1 position  
32 assign g1[1] = g0[1] | (p0[1] & g0[0]);  
33 assign p1[1] = p0[1] & p0[0];  
34  
35 // Position 2: Look back 1 position  
36 assign g1[2] = g0[2] | (p0[2] & g0[1]);  
37 assign p1[2] = p0[2] & p0[1];  
38  
39 // Position 3: Look back 1 position  
40 assign g1[3] = g0[3] | (p0[3] & g0[2]);  
41 assign p1[3] = p0[3] & p0[2];  
42  
43 // Level 2: Span of 4  
44 // Position 0,1: No change  
45 assign g2[0] = g1[0];  
46 assign g2[1] = g1[1];
```

```
47 assign p2[0] = p1[0];
48 assign p2[1] = p1[1];
49
50 // Position 2: Look back 2 positions
51 assign g2[2] = g1[2] | (p1[2] & g1[0]);
52 assign p2[2] = p1[2] & p1[0];
53
54 // Position 3: Look back 2 positions
55 assign g2[3] = g1[3] | (p1[3] & g1[1]);
56 assign p2[3] = p1[3] & p1[1];
57
58 // Carry computation
59 assign c[0] = cin;
60 assign c[1] = g2[0] | (p2[0] & cin);
61 assign c[2] = g2[1] | (p2[1] & cin);
62 assign c[3] = g2[2] | (p2[2] & cin);
63 assign cout = g2[3] | (p2[3] & cin);
64
65 // Sum computation
66 assign sum[0] = p0[0] ^ c[0];
67 assign sum[1] = p0[1] ^ c[1];
68 assign sum[2] = p0[2] ^ c[2];
69 assign sum[3] = p0[3] ^ c[3];
70
71 endmodule
```

# Testbench

```
1  `timescale 1ns / 1ps
2
3  module kogge_stone_adder_tb;
4
5      reg [3:0] A, B;
6      reg cin;
7      wire [3:0] sum;
8      wire cout;
9
10     // Instantiate the Unit Under Test (UUT)
11     kogge_stone_adder_4bit uut (
12         .A(A),
13         .B(B),
14         .cin(cin),
15         .sum(sum),
16         .cout(cout)
17     );
18
19     initial begin
20         $monitor("A=%b, B=%b, cin=%b => sum=%b, cout=%b", A, B, cin, sum, cout);
21
22         A = 4'b0000; B = 4'b0000; cin = 0; #10;
23         A = 4'b0011; B = 4'b0101; cin = 0; #10;
24         A = 4'b1010; B = 4'b1100; cin = 1; #10;
25         A = 4'b1111; B = 4'b1111; cin = 0; #10;
26         A = 4'b1001; B = 4'b0110; cin = 1; #10;
27
28         #10 $finish;
29     end
30
31 endmodule

32 module tb_kogge_stone_adder;
33
34     reg clk;
35     reg rst;
36     reg [3:0] a_in;
37     reg [3:0] b_in;
38     reg cin_in;
39     wire [3:0] sum_out;
40     wire cout_out;
41
42     // Instantiate the top module
43     kogge_stone_top uut (
44         .clk(clk),
45         .rst(rst),
46         .a_in(a_in),
47         .b_in(b_in),
48         .cin_in(cin_in),
49         .sum_out(sum_out),
50         .cout_out(cout_out)
51     );
52
53     // Clock generation
54     initial begin
55         clk = 0;
56         forever #5 clk = ~clk; // 10ns period
57     end
58
59     // Test stimulus
60     initial begin
61         $dumpfile("kogge_stone_adder.vcd");
62         $dumpvars(0, tb_kogge_stone_adder);
```



```

64 // Initialize
65 rst = 1;
66 a_in = 4'b0000;
67 b_in = 4'b0000;
68 cin_in = 1'b0;
69
70 // Reset
71 #10;
72 rst = 0;
73 #10;
74
75 // Test cases
76 $display("Starting Kogge-Stone Adder Tests");
77 $display("Time\tA\tB\tCin\tSum\tCout\tExpected");
78
79 // Test case 1: 0 + 0 + 0 = 0
80 a_in = 4'b0000; b_in = 4'b0000; cin_in = 1'b0;
81 #20;
82 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
83
84 // Test case 2: 1 + 1 + 0 = 2
85 a_in = 4'b0001; b_in = 4'b0001; cin_in = 1'b0;
86 #20;
87 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
88
89 // Test case 3: 5 + 3 + 1 = 9
90 a_in = 4'b0101; b_in = 4'b0011; cin_in = 1'b1;
91 #20;
92 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
93
94
95 a_in = 4'b0111; b_in = 4'b1000; cin_in = 1'b0;
96 #20;
97 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
98 // Test case 5: 15 + 15 + 1 = 31 (overflow case)
99 a_in = 4'b1111; b_in = 4'b1111; cin_in = 1'b1;
100 #20;
101 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
102 // Test case 6: 9 + 6 + 0 = 15
103 a_in = 4'b1001; b_in = 4'b0110; cin_in = 1'b0;
104 #20;
105 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
106 // Test case 7: 12 + 4 + 1 = 17 (overflow)
107 a_in = 4'b1100; b_in = 4'b0100; cin_in = 1'b1;
108 #20;
109 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
110 // Test case 8: 0 + 15 + 1 = 16 (overflow)
111 a_in = 4'b0000; b_in = 4'b1111; cin_in = 1'b1;
112 #20;
113 $display("%0t\t%b\t%b\t%b\t%b\t%b\t%d", $time, a_in, b_in, cin_in, sum_out, cout_out, a_in + b_in + cin_in);
114
115 $display("Test completed");
116 #20;
117 $finish;
118 end
119 // Monitor changes
120 initial begin
121     $monitor("At time %t: A=%b B=%b Cin=%b -> Sum=%b Cout=%b",
122             $time, a_in, b_in, cin_in, sum_out, cout_out);
123 end
124
125 endmodule

```


# Top Module

```
1 module kogge_stone_top (  
2     input wire clk,  
3     input wire rst,  
4     input wire [3:0] a_in,  
5     input wire [3:0] b_in,  
6     input wire cin_in,  
7     output wire [3:0] sum_out,  
8     output wire cout_out  
9 );  
10  
11     // Input registers  
12     wire [3:0] a_reg, b_reg;  
13     wire cin_reg;  
14  
15     // Output registers  
16     reg [3:0] sum_reg;  
17     reg cout_reg;  
18  
19     // Input D Flip-Flops  
20     dff dff_a0 (.clk(clk), .rst(rst), .d(a_in[0]), .q(a_reg[0]));  
21     dff dff_a1 (.clk(clk), .rst(rst), .d(a_in[1]), .q(a_reg[1]));  
22     dff dff_a2 (.clk(clk), .rst(rst), .d(a_in[2]), .q(a_reg[2]));  
23     dff dff_a3 (.clk(clk), .rst(rst), .d(a_in[3]), .q(a_reg[3]));  
24  
25     dff dff_b0 (.clk(clk), .rst(rst), .d(b_in[0]), .q(b_reg[0]));  
26     dff dff_b1 (.clk(clk), .rst(rst), .d(b_in[1]), .q(b_reg[1]));  
27     dff dff_b2 (.clk(clk), .rst(rst), .d(b_in[2]), .q(b_reg[2]));  
28     dff dff_b3 (.clk(clk), .rst(rst), .d(b_in[3]), .q(b_reg[3]));  
29  
30     dff dff_cin (.clk(clk), .rst(rst), .d(cin_in), .q(cin_reg));  
31  
32     // Adder core  
33     wire [3:0] sum_wire;  
34     wire cout_wire;  
35  
36     kogge_stone_4bit adder_core (  
37         .a(a_reg),  
38         .b(b_reg),  
39         .cin(cin_reg),  
40         .sum(sum_wire),  
41         .cout(cout_wire)  
42     );  
43  
44     // Output D Flip-Flops  
45     dff dff_sum0 (.clk(clk), .rst(rst), .d(sum_wire[0]), .q(sum_out[0]));  
46     dff dff_sum1 (.clk(clk), .rst(rst), .d(sum_wire[1]), .q(sum_out[1]));  
47     dff dff_sum2 (.clk(clk), .rst(rst), .d(sum_wire[2]), .q(sum_out[2]));  
48     dff dff_sum3 (.clk(clk), .rst(rst), .d(sum_wire[3]), .q(sum_out[3]));  
49  
50     dff dff_cout (.clk(clk), .rst(rst), .d(cout_wire), .q(cout_out));  
51  
52 endmodule
```

# 4-bit D FlipFlop

```
1  `timescale 1ns / 1ps
2
3  module kogge_stone_pipelined_4bit (
4      input clk,
5      input [3:0] A, B,
6      input cin,
7      output reg [3:0] sum,
8      output reg cout
9  );
10
11  reg [3:0] G, P;
12  reg [3:0] C;
13
14  always @(posedge clk) begin
15      G <= A & B;
16      P <= A ^ B;
17
18      C[0] <= cin;
19      C[1] <= G[0] | (P[0] & C[0]);
20      C[2] <= G[1] | (P[1] & G[0]) | (P[1] & P[0] & C[0]);
21      C[3] <= G[2] | (P[2] & G[1]) | (P[2] & P[1] & G[0]) | (P[2] & P[1] & P[0] & C[0]);
22
23      sum <= P ^ C;
24      cout <= G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) | (P[3] & P[2] & P[1] & G[0]) | (P[3] & P[2] & P[1] & P[0] & C[0]);
25  end
26
27  endmodule
```

# Reports

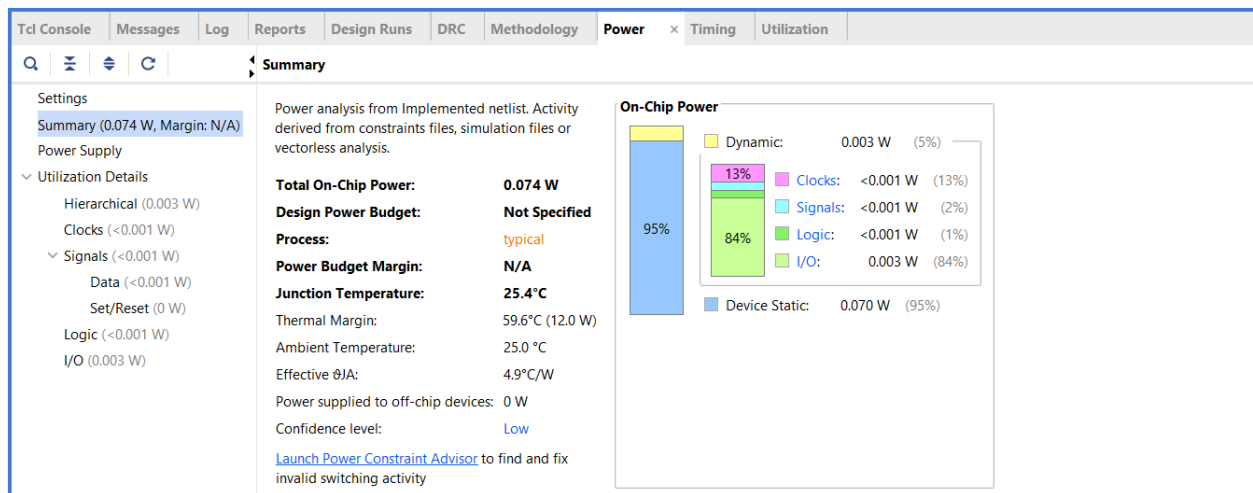

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPowerTimingUtilization?

</

Tcl Console	Messages	Log	Reports	Design Runs	DRC	Methodology	Power	Timing	Utilization	
Check Timing										
General Information	Timer Settings	Design Timing Summary	Clock Summary (1)	Methodology Summary (15)	> Check Timing (15)	▼ Intra-Clock Paths	▼ clk	Setup 8.019 ns (5)	Hold 0.234 ns (5)	Pulse Width 4.500 ns (30)
Inter-Clock Paths	Other Path Groups	User Ignored Paths	> Unconstrained Paths							
Timing Check	Count	Worst Severity								
no_input_delay	10	High								
no_output_delay	5	High								
no_clock	0									
constant_clock	0									
pulse_width_clock	0									
unconstrained_internal_endpoints	0									
multiple_clock	0									
generated_clocks	0									
loops	0									
partial_input_delay	0									
partial_output_delay	0									
latch_loops	0									

Tcl Console	Messages	Log	Reports	Design Runs	DRC	Methodology	Power	Timing	Utilization	
Hierarchy										
Hierarchy	Summary	▼ Slice Logic	▼ Slice LUTs (<1%)	LUT as Logic (<1%)	▼ Slice Registers (<1%)	Register as Flip Flop (<1%)	▼ Slice Logic Distribution	▼ Slice (<1%)	SLICEL	▼ Slice Registers (<1%)
Register driven from wi										
Name	Slice LUTs (32600)	Slice Registers (65200)	Slice (8150)	LUT as Logic (32600)	Bonded IOB (210)	BUFCTRL (32)				
kogge_stone_top	4	14	2	4	16	1				
dff_a0 (dff)	1	1	2	1	0	0				
dff_a1 (dff_0)	0	1	1	0	0	0				
dff_a2 (dff_1)	1	1	1	1	0	0				
dff_a3 (dff_2)	0	1	1	0	0	0				
dff_b0 (dff_3)	0	1	1	0	0	0				
dff_b1 (dff_4)	0	1	1	0	0	0				
dff_b2 (dff_5)	0	1	1	0	0	0				
dff_b3 (dff_6)	0	1	1	0	0	0				
dff_cin (dff_7)	2	1	2	2	0	0				